

As we'll derive in recitation, the equation for the current $I(t)$ in terms of the potential $V(t)$ is the second-order linear constant coefficient equation

$$I''(t) + (R/L) I'(t) + (1/CL) I(t) = V'(t)$$

where R , C and L are the resistance, capacitance, and inductance respectively.

Let's look at this in a few simple cases. We'll start with $V'(t) = 0$, so we have a constant potential established. Think of a battery running the circuit. Then our equation reduces to

$$I''(t) + (R/L) I'(t) + (1/CL) I(t) = 0$$

In the case when the resistance is zero (an idealized case where we have no loss due to heat), this simplifies even further to


$$I''(t) + (1/CL) I(t) = 0$$

This should look very familiar - it's the equation for oscillatory motion. Its plot is sinusoidal and corresponds to oscillatory motion of the current, sloshing back and forth through the circuit. Here are some examples; in the first, $R = 1$, $L = 2$, $C = 3$; in the second, $R = 1/10$.

In[6]:= `DSolve[{J''[t] + (1/2) J'[t] + (1/6) J[t] == 0, J[0] == 1, J'[0] == 0}, J, t]`

Out[6]:= `{ {J -> Function[{t}, (1/5) e^{-t/4} (5 Cos[1/4 sqrt(5/3) t] + sqrt(15) Sin[1/4 sqrt(5/3) t])] } }`

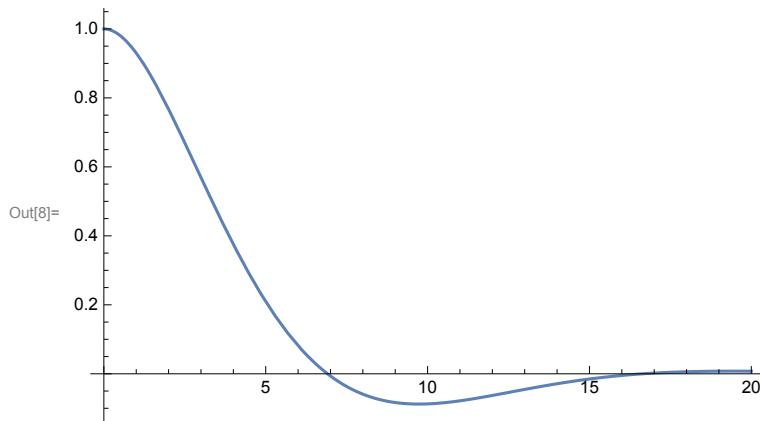In[8]:= `Plot[1/5 e^{-t/4} (5 Cos[1/4 sqrt(5/3) t] + sqrt(15) Sin[1/4 sqrt(5/3) t]), {t, 0, 20}]`




(* Example of large resistance and lots of damping. *)

In[9]:= `DSolve[{J''[t] + (1/20) J'[t] + (1/6) J[t] == 0, J[0] == 1, J'[0] == 0}, J, t]`

Out[9]:= `{ {J -> Function[{t}, (1/797) e^{-t/40} (797 Cos[1/40 sqrt(797/3) t] + sqrt(2391) Sin[1/40 sqrt(797/3) t])] } }`
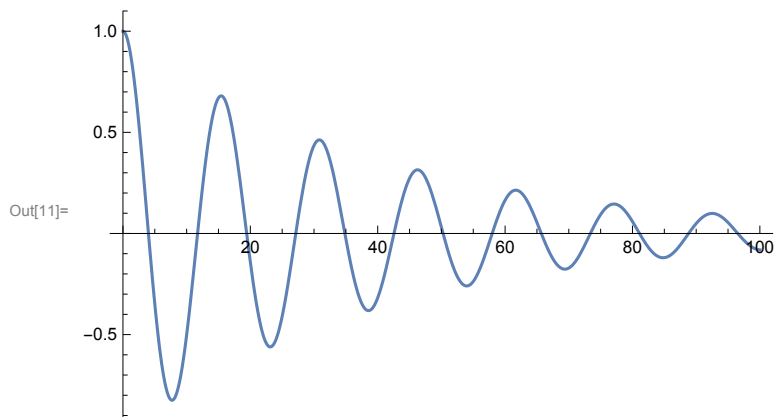
```
In[11]:= Plot[ $\frac{1}{797} e^{-t/40} \left( 797 \cos\left[\frac{1}{40} \sqrt{\frac{797}{3}} t\right] + \sqrt{2391} \sin\left[\frac{1}{40} \sqrt{\frac{797}{3}} t\right] \right)$ , {t, 0, 100}]
```



(* Smaller resistance *)


```
In[12]:= DSolve[{J''[t] + (10/2) J'[t] + (1/6) J[t] == 0, J[0] == 1, J'[0] == 0}, J, t]
```

```
Out[12]= {{J -> Function[{t},
```

$$\frac{1}{146} \left(73 e^{\left(-\frac{5}{2} - \frac{\sqrt{73}}{2}\right) t} - 5 \sqrt{219} e^{\left(-\frac{5}{2} - \frac{\sqrt{73}}{2}\right) t} + 73 e^{\left(-\frac{5}{2} + \frac{\sqrt{73}}{2}\right) t} + 5 \sqrt{219} e^{\left(-\frac{5}{2} + \frac{\sqrt{73}}{2}\right) t} \right)]}}$$

```
In[15]:= Plot[
```
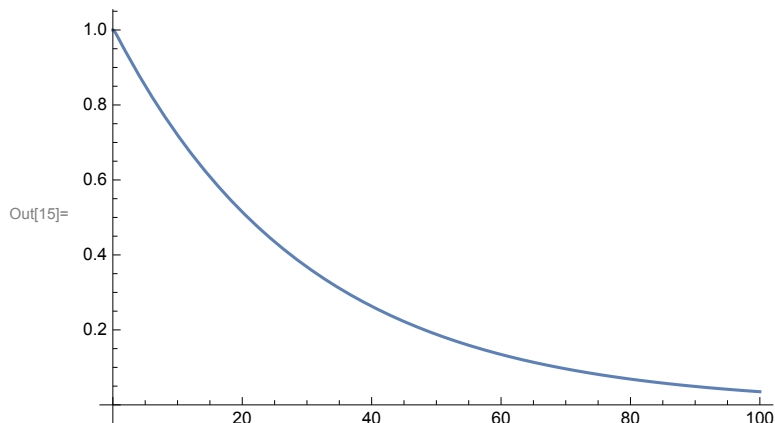
$$\frac{1}{146} \left(73 e^{\left(-\frac{5}{2} - \frac{\sqrt{73}}{2}\right) t} - 5 \sqrt{219} e^{\left(-\frac{5}{2} - \frac{\sqrt{73}}{2}\right) t} + 73 e^{\left(-\frac{5}{2} + \frac{\sqrt{73}}{2}\right) t} + 5 \sqrt{219} e^{\left(-\frac{5}{2} + \frac{\sqrt{73}}{2}\right) t} \right), \{t, 0, 100\}]$$



(* Huge resistance - overdamping *)


Now let's look at the case where we introduce a non-zero voltage, like an oscillator. For simplicity, let's take $R = 0$ to start and use a pure oscillator like $V(t) = \sin(2t)$.

```
In[16]:= DSolve[{J''[t] + (0) J'[t] + J[t] == Sin[2 t], J[0] == 1, J'[0] == 0}, J, t]
```

```
Out[16]= {{J -> Function[{t},
  1/6 (6 Cos[t] + 4 Sin[t] - 3 Cos[t] Sin[t] - Cos[3 t] Sin[t] - 4 Cos[t] Sin[t]^3)]}}
```

```
In[17]:= Plot[
```
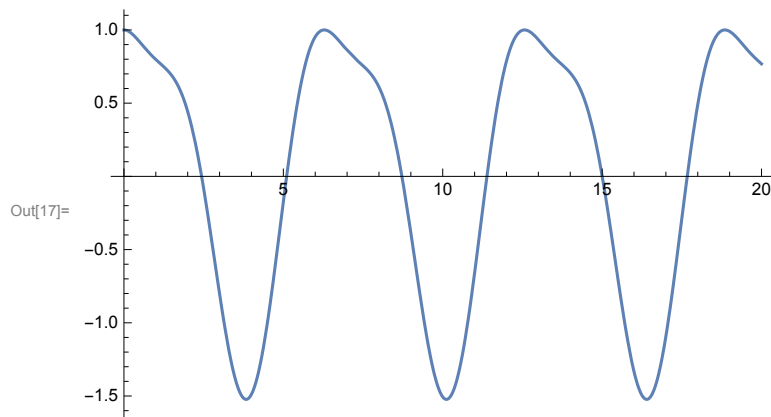
```
  1/6 (6 Cos[t] + 4 Sin[t] - 3 Cos[t] Sin[t] - Cos[3 t] Sin[t] - 4 Cos[t] Sin[t]^3), {t, 0, 20}]
```



```
In[37]:= DSolve[
```


```
  {J''[t] + (0) J'[t] + J[t] == (Cos[2 t] + 3) E^(-t/10), J[0] == 1, J'[0] == 0}, J, t]
```

```
Out[37]= {{J -> Function[{t},
  - 1/91001 e^(-t/10) (149399 e^(t/10) Cos[t] - 225250 Cos[t]^2 - 15150 Cos[t] Cos[3 t] -
  32040 e^(t/10) Sin[t] + 9010 Cos[t] Sin[t] + 505 Cos[3 t] Sin[t] -
  315350 Sin[t]^2 - 505 Cos[t] Sin[3 t] - 15150 Sin[t] Sin[3 t])]]}}
```

```
In[39]:= Plot[-  $\frac{1}{91001} e^{-t/10} (149399 e^{t/10} \cos[t] - 225250 \cos[t]^2 - 15150 \cos[t] \cos[3t] -$   

 $32040 e^{t/10} \sin[t] + 9010 \cos[t] \sin[t] + 505 \cos[3t] \sin[t] -$   

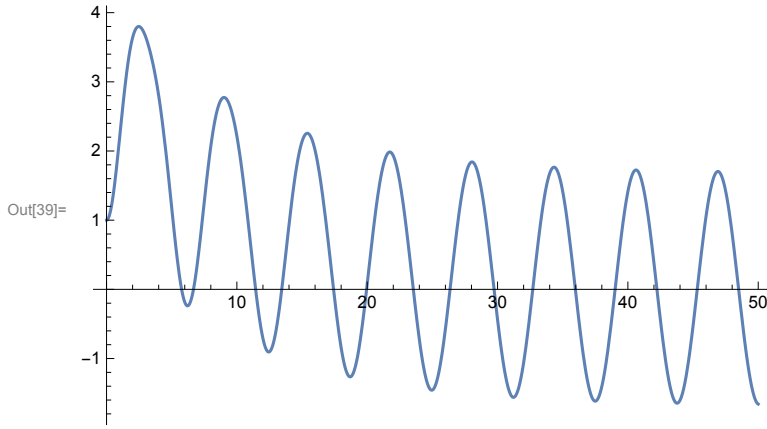 $315350 \sin[t]^2 - 505 \cos[t] \sin[3t] - 15150 \sin[t] \sin[3t])$ , {t, 0, 50}]
```




(* Here, the oscillation does some funny stuff at the beginning,
 and then dies out as time goes on -
 we return to a purely oscillatory solution *)

```
In[40]:= DSolve[{J''[t] + (0) J'[t] + J[t] == Cos[t], J[0] == 1, J'[0] == 0}, J, t]
```

```
Out[40]:= {{J -> Function[{t},  $\frac{1}{4} (2 \cos[t] + 2 \cos[t]^3 + 2 t \sin[t] + \sin[t] \sin[2 t])$ ]}}
```
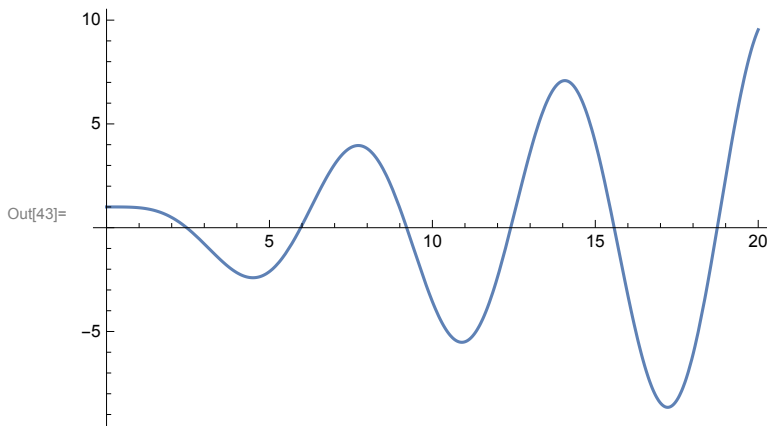
```
In[43]:= Plot[ $\frac{1}{4} (2 \cos[t] + 2 \cos[t]^3 + 2 t \sin[t] + \sin[t] \sin[2 t])$ , {t, 0, 20}]
```




(* Here we have resonance -
 the current feeds back and increases itself over time, blowing up in strength *)

```
In[46]:= DSolve[{J''[t] + (0) J'[t] + J[t] == Cos[(120/100) t], J[0] == 1, J'[0] == 0}, J, t]
```

```
Out[46]:= {{J -> Function[{t},  $\frac{1}{22} \left( 72 \cos[t] - 55 \cos\left[\frac{t}{5}\right] \cos[t] + 5 \cos[t] \cos\left[\frac{11t}{5}\right] + 55 \sin\left[\frac{t}{5}\right] \sin[t] + 5 \sin[t] \sin\left[\frac{11t}{5}\right] \right)$ ]}}
```
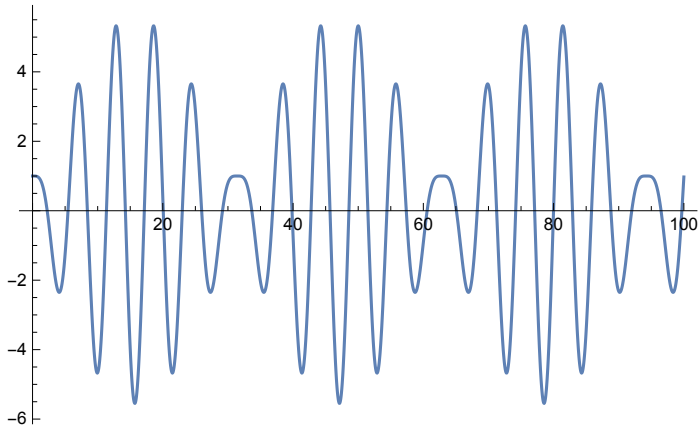
```
In[47]:= Plot[ $\frac{1}{22} \left( 72 \cos[t] - 55 \cos\left[\frac{t}{5}\right] \cos[t] + 5 \cos[t] \cos\left[\frac{11t}{5}\right] + 55 \sin\left[\frac{t}{5}\right] \sin[t] + 5 \sin[t] \sin\left[\frac{11t}{5}\right] \right)$ , {t, 0, 100}]
```



(* Here we see beats that continue periodically. Here's another plot over long time: *)

```
In[49]:= Plot[ $\frac{1}{22} \left( 72 \cos[t] - 55 \cos\left[\frac{t}{5}\right] \cos[t] + 5 \cos[t] \cos\left[\frac{11t}{5}\right] + 55 \sin\left[\frac{t}{5}\right] \sin[t] + 5 \sin[t] \sin\left[\frac{11t}{5}\right] \right)$ , {t, 0, 500}]
```

